 




PAMANTASAN NG LUNGSOD NG MAYNILA
(University of the City of Manila)
Intramuros, Manila

Microprocessor Lab

Laboratory Activity No. 1
Familiarization with TinkerCAD



Score

Submitted by:
Antifona, Jedlyn D.
<1:00 pm – 7:00 pm> / <CpE 412-2>

Date Submitted
16-09-2023


Submitted to:
Engr. Maria Rizette H. Sayo

1. Exercise

- A process in Tinkercad where we can develop electronic circuits that can be quickly updated, modified and tested is called **prototyping process**.
- In Tinkercad, **the Start/Stop Simulation** tests the working of the circuits and the components.
- The device used to assemble and connect the various components is known as **Breadboard**.
- In an electronic circuit with LED, the positive end of the circuit should be connected to **Anode** and negative end should be connected to **Cathode** of the LED.
- A **Resistor** is used to restrict the flow of current to electrical components

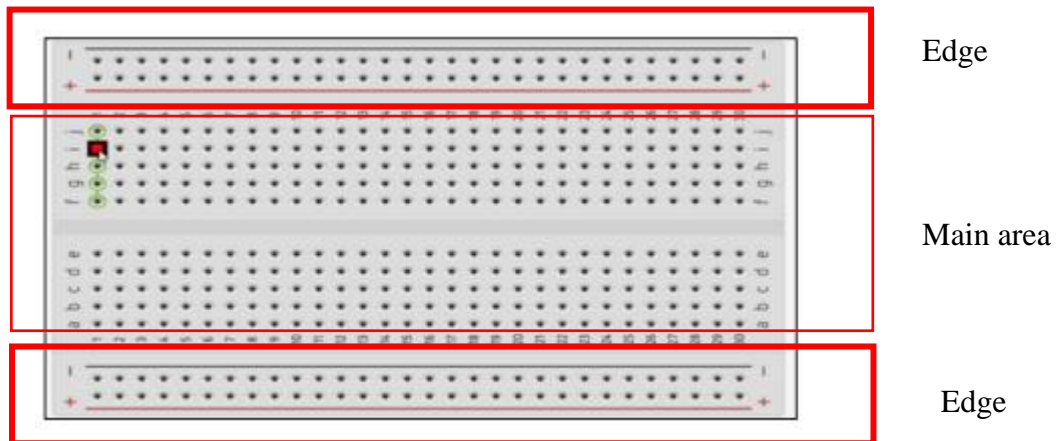2. Label the following:

- Anode and Cathode in a LED
- Different parts of breadboard



- List the electronic components used in a circuit assembly

Arduino Uno
Breadboard
Jumper Wire
LED
Resistor 1k ohm
Potentiometer